

## **S-Parameters and Power Gain Definitions**

### **Disclaimer**

**The Author makes no representation or warranties with respect to the accuracy or completeness of the contents of this document and specifically disclaims any implied warranties of merchantability or fitness for any particular purpose and shall in no event be liable for any loss of profit or any other commercial damage, including but not limited to special, incidental, consequential or other damages.**

## S-Parameters and Power Gain Definitions

### Contents

1	S-Parameters Revision	3
1.1	The S-Parameters for a General 2 Port Network	3
1.2	Power Waves and S-Parameter Definitions	5
1.3	Complex and Average and Power	7
1.3.1	Useful Complex Relationships	7
1.4	Bi-directional Power Along a Transmission Line	10
1.5	Unilateral and Bilateral Properties of the Network	11
2	Power Gain Definitions	13
2.1	Operating Power Gain	13
2.2	Available Power Gain	16
2.3	Transducer Power Gain	17
2.4	Comparing the Power Gain Definitions	17
2.5	Power Gains in Practical Systems	18
2.5.1	Matching for Maximum Power Transfer	19
3	References	21

### Figures

Figure 1-1	Some general 2 port network connected to an arbitrary source and load	4
Figure 1-2	The 2-port network connections showing the power definitions	7
Figure 2-1	A schematic showing two ways of substituting a 2-port network into a cascade: unmatched (a) and simultaneously conjugately matched (b)	19
Figure 2-2	A generic 2-port network that is simultaneously conjugately matched to a source and load	20

### 1 S-Parameters Revision

#### 1.1 The S-Parameters for a General 2 Port Network


Suppose we have a 2 port network whose S parameters we have measured accurately on a vector network analyzer (VNA) across some frequency range of interest. By a 2 port 'network' we mean almost any RF device that has 2 ports, with suitable connectors, that we can safely measure on the VNA using the 'full 2 ports' calibration and we will assume that it gives reliable S-parameter values. We will also refer to it as 'device under test' (DUT). In other words, it contains linear components, for example resistors, inductors and capacitors. It can be an amplifier and contain non-linear devices such as transistors and diodes but, as a whole *the network must be operating linearly*. If it is an amplifier, it must be working in the linear region of its transfer characteristic. It must not work at such a high signal level that it is into compression and not at such a low signal level that might be below the background noise.

The linear requirement applies to the VNA as well. Most VNAs will have quite a good dynamic range but it is very easy to exceed the maximum input power allowed into the VNA. All VNAs will have some means of adjusting the (incident) power level that is used for the measurement and some thought is needed about what value to set this to before performing the measurement. For example, if the VNA has + 10 dBm maximum input power, a good rule of thumb is to arrange for the maximum expected VNA input power to be around 10 dB less than this, or 0 dBm. If we are measuring an amplifier for example, we must have at least some idea of its gain and output 1 dB compression point (P1dB). The P1dB is, by definition, 1 dB into non-linearity so we need to comfortably avoid this. If its P1dB is 0 dBm and we expect a gain of about 20 dB then, applying – 20 dBm at the amplifier input might be safe for the VNA but take the amplifier itself into compression so it would be safer to reduce (back off) the input by say another 10 dB to – 30 dBm. Most amplifiers go into compression over a more abrupt window than 10 dB and this level should normally be comfortably into the linear part of the characteristic.

Finally we will assume that we have assigned its ports correctly as '1' and '2' related to the VNA connections when the measurements were made. That should have been clear from the markings on the VNA, normally port 1 on the VNA connects to what we define as port 1 on the DUT and similarly with port 2. There is no rule about which port on the VNA should be connected to which actual port on the DUT as long as we know which ports were in fact connected. Then we can correctly relate the measurements made to the DUT. Having said that, if we are measuring a non-reciprocal device such as an amplifier, for which power is intended to travel in one direction only, it is very common to make port 1 the input port and port 2 the output port. We should be comfortable with any sort of port definitions.

Actually we are not going to dwell too long on VNA measurements but we will look at the S-parameter results themselves and what can be done with them in connection with power gains in particular. Plenty of such information on VNA measurements is available from VNA manufacturer's application notes like those from Agilent [4][5]. Now let us assume that we have a good set of S-parameters for this network and let us connect it to an arbitrary source and load as shown in Figure 1-1.

## S-Parameters and Power Gain Definitions

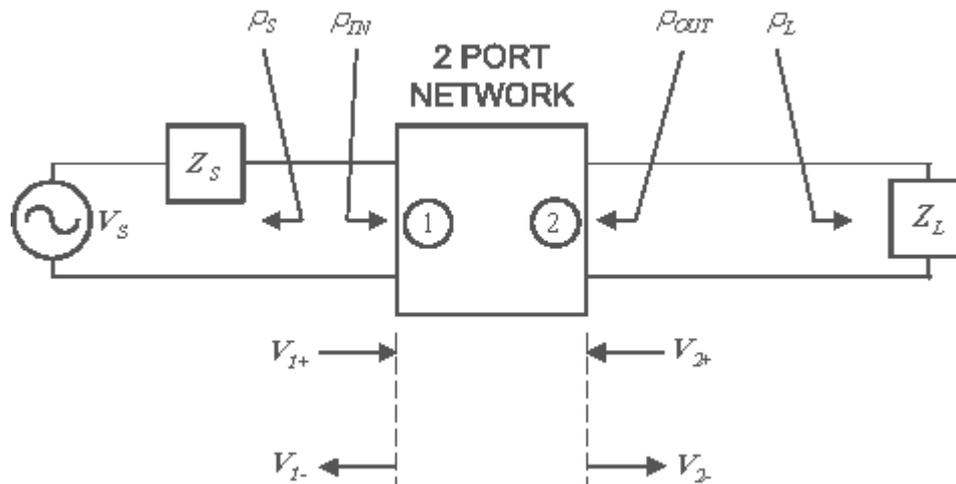

**Figure 1-1 Some general 2 port network connected to an arbitrary source and load**

Figure 1-1 schematically shows the 2 port network of interest connected to an arbitrary source on the left, which is represented by a Thevenin equivalent circuit, and an arbitrary load on the right. We will generically refer to it as a *network* but it could be an amplifier, attenuator, filter or anything else for which we have a reliable set of S-parameter measurements. The ports have been named 1 and 2 as shown for convenience and, in this case, we are considering port 1 to be the input and port 2 the output. As mentioned earlier, it does not matter how we number the ports but we do need some sort of referencing system to ensure that we keep track of things. The port numbers we actually choose will relate to the indices of the S-parameter matrix elements, as we shall see later.

Remember that, unless stated otherwise, all values are complex quantities because they are all amplitude and phase sensitive. This applies to all of the electrical quantities: voltages, reflection coefficients, impedances, gains, losses. It may even be applied to power, but we are mostly only interested in the real part. In the complex algebra which follows, it is essential that we keep track of which quantities are complex and which are just magnitudes or real values, as they have completely different meanings. It is safe to assume that any value expressed in between vertical bars will be a magnitude and all other values will be complex.

Although we don't usually want them to, all of these values will change to some extent with frequency so whenever an S-parameter or any of the other parameters are defined so should the associated frequency. Unless mentioned otherwise, we will assume that all of the parameters have been measured at the same frequency.

Assume the following:

$Z_s$  is the source impedance.

$Z_L$  is the load impedance.

$\rho_s$  is the reflection coefficient looking into the source.

$\rho_L$  is the reflection coefficient looking into the load.

$\rho_{IN}$  is the reflection coefficient looking into port 1 of the network.

$\rho_{OUT}$  is the reflection coefficient looking into port 2 of the network.

$V_{1+}$  is the voltage wave incident at port 1.

$V_{1-}$  is the voltage wave reflected at port 1.

$V_{2+}$  is the voltage wave incident at port 2.

## S-Parameters and Power Gain Definitions

$V_{2-}$  is the voltage wave reflected at port 2.

The reflection coefficient at a port is defined as the reflected complex voltage divided by the incident complex voltage, so the reflection coefficient itself is also complex. Therefore, each of the following reflection coefficients is defined as follows:

$$\rho_{IN} = \frac{V_{1-}}{V_{1+}} \quad (1.1)$$

$$\rho_{OUT} = \frac{V_{2-}}{V_{2+}} \quad (1.2)$$

For  $\rho_S$  and  $\rho_L$ , remember that we have defined the incident and reflected voltages relative to the ports of the network, not to those on the source or the load, therefore:

$$\rho_S = \frac{V_{1+}}{V_{1-}} = \frac{1}{\rho_{IN}} \quad (1.3)$$

$$\rho_L = \frac{V_{2+}}{V_{2-}} = \frac{1}{\rho_{OUT}} \quad (1.4)$$

The convention for the forward and reflected voltages will be clear from the diagram. The subscript is associated with the port, 1 or 2 and includes a plus sign (+) if the wave is entering the port or a negative sign (-) if the wave is emerging from the port.

### 1.2 Power Waves and S-Parameter Definitions

For an  $n$ -port network, the scattering or S-parameter matrix is an  $n$  by  $n$  matrix. In our case the network has 2 ports so  $n = 2$  and we will denote the associated S-parameter matrix by the uppercase letter 'S' in bold italic,  $\mathbf{S}$ . Regular type will be used for each of the elements within the matrix. Therefore,

$$\mathbf{S} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \quad (1.5)$$

With S-parameters it is useful to deal with quantities which are known as power waves. These are related to the forward and reverse voltages at each of the ports, normalised by the square root of the system impedance. They are still complex quantities, despite their name. We use the lower case letter  $a$  to denote a power wave incident at a port and the lower case letter  $b$  for a power wave that is reflected from a port. In each case we include a subscript according to the port number. So, for example  $a_1$  is the power wave incident at port 1 and  $b_2$  is the power wave reflected from port 2. For the 2 port network, the power waves are related to the incident and reflected voltages at each of the ports as follows:

$$a_1 = \frac{V_{1+}}{\sqrt{Z_0}} \quad (1.6)$$

$$a_2 = \frac{V_{2+}}{\sqrt{Z_0}} \quad (1.7)$$

## S-Parameters and Power Gain Definitions

$$b_1 = \frac{V_{1-}}{\sqrt{Z_0}} \quad (1.8)$$

$$b_2 = \frac{V_{2-}}{\sqrt{Z_0}} \quad (1.9)$$

The following matrix defines the 2 port S-parameter matrix in terms of power waves.

$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \quad (1.10)$$

Multiplying out the matrices gives

$$b_1 = S_{11}a_1 + S_{12}a_2 \quad (1.11)$$

and

$$b_2 = S_{21}a_1 + S_{22}a_2 \quad (1.12)$$

(1.11) and (1.12) are used to define the individual S-parameter matrix elements as follows:

- $S_{11}$  is defined with  $a_2 = 0$ , so

$$S_{11} = \frac{b_1}{a_1} \quad (1.13)$$

- $S_{12}$  is defined with  $a_1 = 0$ , so

$$S_{12} = \frac{b_1}{a_2} \quad (1.14)$$

- $S_{21}$  is defined with  $a_2 = 0$ , so


$$S_{21} = \frac{b_2}{a_1} \quad (1.15)$$

- $S_{22}$  is defined with  $a_1 = 0$ , so

$$S_{22} = \frac{b_2}{a_2} \quad (1.16)$$

The required conditions  $a_1 = 0$  and  $a_2 = 0$  may be achieved by terminating the associated port with a high quality load whose impedance is exactly  $Z_0$ . This is the principle used by a vector network analyzer (VNA) to measure S-parameters. The termination could either be the source impedance of a signal generator or a physical load, according to the particular S-parameter being measured. Part of the calibration routine for modern VNAs includes multi-port error correction algorithms, whose purpose is to correct for uncertainties of the source and load impedances themselves.

### 1.3 Complex and Average and Power

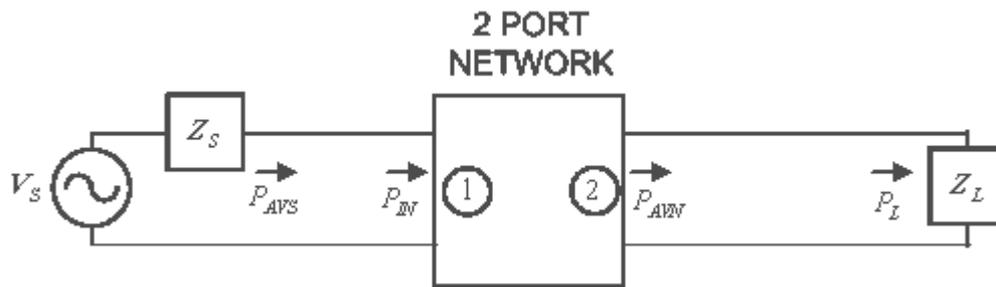

**Figure 1-2 The 2-port network connections showing the power definitions**

Figure 1-2 is a schematic for the same configuration as that shown in Figure 1-1, but in this case it shows the following forward powers:

- Power available from the source,  $P_{AVS}$ .
- Input power to the network,  $P_{IN}$ .
- Power available from the network,  $P_{AVN}$ .
- Power dissipated in the load,  $P_L$ .

These will be used later for the power gain definitions.

To arrive at the power input to the network  $P_{IN}$  we need to find an expression for the average (or mean) power at the same point. Average power is the correct power definition applicable to the power gain definitions that we will be looking at. Average power is calculated by its heating effect averaged over many cycles. As we shall see later, if the power originates from sinusoidal voltage and current waveforms the resulting power waveform will have a period that is half of that of either of the original waveforms, or twice the frequency. There are many other definitions of power, in particular *peak power* which we will look at another time. Please refrain from using the term root mean square (RMS) power or ‘RMS power’ which is sometimes erroneously used to refer to average power. If you have a power waveform you can indeed calculate an RMS value for it as an exercise in mathematics and call it RMS power but in is not very useful. People who use this expression generally mean average power as derived from sinusoidal voltages and/or currents, each of which has an RMS value. Lets get back to our main theme and think about some complex expressions which will become useful later.

#### 1.3.1 Useful Complex Relationships

If  $A$  is any complex number, for example expressed in rectangular form as  $A = x + jy$ , then it is easy to verify that

$$\text{Re}(A) = \frac{1}{2}(A + A^*) \quad (1.17)$$

where  $\text{Re}(\ )$  means ‘real part of’ and the asterisk superscript means ‘complex conjugate of’, or  $A^* = x - jy$ .

If  $B$  is another complex number then for the product of the real parts of each of the complex numbers  $A$  and  $B$  is given by

## S-Parameters and Power Gain Definitions

$$\begin{aligned}
 \operatorname{Re}(A)\operatorname{Re}(B) &= \frac{1}{4}(A + A^*)(B + B^*) \\
 &= \frac{1}{4}(A^*B + AB) + \frac{1}{4}(AB^* + A^*B^*) \\
 &= \frac{1}{2}\operatorname{Re}(A^*B + AB)
 \end{aligned} \tag{1.18}$$

(1.18) is true because

$$(AB^* + AB)^* = A^*B + A^*B^* \tag{1.19}$$

It is understood that the magnitude of a complex number  $|A|$  can be inferred from Pythagoras's theorem applied to the magnitudes of its real and imaginary components which, by definition, are at right angles, so that if  $A = x + jy$ , then

$$\begin{aligned}
 |A| &= \sqrt{x^2 + y^2} \\
 |A|^2 &= x^2 + y^2
 \end{aligned} \tag{1.20}$$

Another useful relationship is that the magnitude squared of a complex number is the product of the complex number itself and its conjugate, so

$$AA^* = |A|^2 \tag{1.21}$$

This may be verified by sketching vectors for a complex number and its conjugate on an argand diagram. Both will have the same magnitude.

Whilst we are on the subject, if we have two complex numbers  $A$  and  $B$  such that

$$A = x + jy \tag{1.22}$$

and

$$B = p + jq \tag{1.23}$$

Then some complex arithmetic will confirm the following relationships

$$\begin{aligned}
 |AB| &= |A||B| \\
 \frac{|A|}{|B|} &= \frac{|A|}{|B|}
 \end{aligned} \tag{1.24}$$

Returning to Figure 1-1, we can use (1.18) to calculate the real power  $W$  at port 1, the input to the network, arising from the *total input voltage*  $V_1$  (without any + or – sign in the subscript). The input total voltage is the voltage that results from the complex sum of the forward (or incident) voltage  $V_{1+}$  and the reflected voltage  $V_{1-}$ , so

## S-Parameters and Power Gain Definitions

$$\begin{aligned}
 W &= \frac{[\operatorname{Re}(V_1)]^2}{Z_0} \\
 &= \frac{1}{2Z_0} \operatorname{Re}(V_1 V_1^* + V_1^2) \\
 &= \frac{1}{2Z_0} \operatorname{Re}(|V_1|^2 + V_1^2)
 \end{aligned} \tag{1.25}$$

The expression for  $W$  contains the constant value  $|V_1|^2$  which is the square of the amplitude of the total input voltage of the network. As a sinusoidal (strictly co-sinusoidal) function of time in exponential form,  $V_1$  could be expressed as

$$V_1 = \hat{V}_1 \cos \omega t \tag{1.26}$$

Using Euler's identity [9] for a general variable  $x$  of the form

$$e^{jx} = \cos x + j \sin x \tag{1.27}$$

Then

$$\begin{aligned}
 V_1 &= \hat{V}_1 \cos \omega t \\
 &= \operatorname{Re}(\hat{V}_1 \cos \omega t + j \hat{V}_1 \sin \omega t) \\
 &= \operatorname{Re}(\hat{V}_1 e^{j\omega t})
 \end{aligned} \tag{1.28}$$

where

$V_1$  is the *instantaneous* value of the sinusoidal voltage

$\hat{V}_1$  is the peak value (or amplitude) of the voltage

$\omega = 2\pi f$  is the angular frequency of the source in radian per seconds (rad/s), and

$f$  is the frequency in Hertz (Hz).

In electrical engineering it is generally understood that the real part operator may be omitted and the sinusoidal waveform may simply be expressed as

$$V_1 = \hat{V}_1 e^{j\omega t} \tag{1.29}$$

The amplitude of the sinusoidal voltage may alternatively be expressed as a magnitude in the form  $|V_1|$ , therefore

$$V_1 = |V_1| e^{j\omega t} \tag{1.30}$$

From (1.25) the term  $V_1^2$  is given by squaring the expression in (1.30), that is

$$V_1^2 = |V_1|^2 e^{j2\omega t} \tag{1.31}$$

This represents a cosine wave at twice the fundamental frequency. Like any sine or cosine wave, it will have a mean of zero over many cycles. For the average power  $W_{MEAN}$  therefore may be given by either of the following expressions.

## S-Parameters and Power Gain Definitions

$$\begin{aligned}
 W_{MEAN} &= \frac{1}{2Z_0} \operatorname{Re}(VV^*) = \frac{|V|^2}{2Z_0} \\
 &= \frac{1}{2} Z_0 \operatorname{Re}(II^*) = \frac{Z_0}{2} |I|^2 \\
 &= \frac{1}{2} \operatorname{Re}(VI^*) = \frac{1}{2} |V||I|
 \end{aligned} \tag{1.32}$$

### 1.4 Bi-directional Power Along a Transmission Line

The situation we face with Figure 1-2 at the input to the network is like one of an unmatched transmission line. There will be components of forward and reflected voltages, currents and powers that will create corresponding *instantaneous* voltages, currents and powers. The following equations, based on transmission line theory [10], describe the instantaneous voltage, made up of the forward and reverse voltages; and the total instantaneous current, made up of the forward and reverse currents.

$$V_1 = V_{1+} + V_{1-} \tag{1.33}$$

and

$$\begin{aligned}
 Z_0 I_1 &= V_{1+} - V_{1-} \\
 I_1 &= \frac{1}{Z_0} (V_{1+} - V_{1-})
 \end{aligned} \tag{1.34}$$

The instantaneous power is the product  $V_1 I_1$ . This may be obtained by multiplying (1.33) and (1.34), then substituting expressions for  $V_{1+}$  and  $V_{1-}$  in terms of the forward and reverse power waves,  $a_1$  and  $b_1$  respectively, obtained from (1.6) and (1.8) as follows:

$$\begin{aligned}
 Z_0 V_1 I_1 &= (V_{1+} + V_{1-})(V_{1+} - V_{1-}) \\
 V_1 I_1 &= \frac{1}{Z_0} (V_{1+}^2 - V_{1-}^2) \\
 &= \frac{V_{1+}^2}{Z_0} \left( 1 - \frac{V_{1-}^2}{V_{1+}^2} \right) \\
 &= \frac{V_{1+}^2}{Z_0} (1 - \rho_{IN}^2)
 \end{aligned} \tag{1.35}$$

The last line of (1.35) used the definition of  $\rho_{IN}$  from (1.1). Remembering that the voltages and currents considered in (1.35) are instantaneous values of sinusoidal waveforms, so the product  $V_1 I_1$  is also instantaneous. From the discussions in Section 1.3, this may be converted to a mean power  $P_{IN}$  by using the first line of (1.32) and changing  $V_{1+}$ ,  $V_{1-}$  and therefore  $\rho_{IN}$  to their magnitude values. Therefore

$$P_{IN} = \frac{|V_{1+}|^2}{2Z_0} (1 - |\rho_{IN}|^2) \tag{1.36}$$

### 1.5 Unilateral and Bilateral Properties of the Network

Looking at Figure 1-1 again, consider what might happen to  $\rho_{IN}$  if we changed  $Z_L$  (and therefore  $\rho_L$ ).

If the network was a reasonably high gain amplifier the answer might be ‘not much’ or by some negligible amount. In some cases amplifiers are deliberately designed as ‘buffers’ precisely for this reason. However one of the important advantages of S-parameters is that *they take account of the effects of signals in both directions*. As we know, all such signals are expressed in both amplitude and phase. If we are using S-parameters to design a 2 port network, getting this wrong might make the difference between ending up with a network which is supposed to amplify but oscillates or one that is supposed to be an oscillator but which will not even start oscillating. A perfect buffer amplifier is an example of a unilateral device. More generally, most 2 port devices have at least some bilateral properties which must be taken into account.

Using the definitions of the  $a$  and  $b$  power waves from equations (1.6), (1.7), (1.8) and (1.9) and substituting them into (1.11) and (1.12)

$$V_{1-} = S_{11}V_{1+} + S_{12}V_{2+} \quad (1.37)$$

From (1.4)

$$V_{2+} = \rho_L V_{2-} \quad (1.38)$$

Substituting (1.38) into (1.37):

$$V_{1-} = S_{11}V_{1+} + S_{12}\rho_L V_{2-} \quad (1.39)$$

A similar substitution for  $V_{2-}$  results in

$$V_{2-} = S_{21}V_{1+} + S_{22}\rho_L V_{2-} \quad (1.40)$$

Re-arranging (1.39) in terms of  $V_{2-}$  gives

$$V_{2-} = \frac{V_{1-} - S_{11}V_{1+}}{S_{12}\rho_L} \quad (1.41)$$

Similarly, from (1.40)

$$V_{2-} = \frac{S_{21}V_{1+}}{1 - S_{22}\rho_L} \quad (1.42)$$

Equating (1.41) and (1.42), after some re-arrangement, yields

$$V_{1-} = V_{1+} \left( S_{11} + \frac{S_{12}S_{21}\rho_L}{1 - S_{22}\rho_L} \right) \quad (1.43)$$

Thus

$$\rho_{IN} = \frac{V_{1-}}{V_{1+}} = S_{11} + \frac{S_{12}S_{21}\rho_L}{1 - S_{22}\rho_L} \quad (1.44)$$

## S-Parameters and Power Gain Definitions

A similar argument applied to  $\rho_{OUT}$  gives the following result

$$\rho_{OUT} = \frac{V_{2-}}{V_{2+}} = S_{22} + \frac{S_{12}S_{21}\rho_S}{1 - S_{22}\rho_S} \quad (1.45)$$

Equations (1.44) and (1.45) are very useful and well worth remembering. Equation (1.44) tells us how the reflection coefficient that we see at the input of the network  $\rho_{IN}$  is affected by the output loading. Equation (1.45) describes how the output reflection coefficient  $\rho_{OUT}$  is affected by the source impedance.

Some 2-port devices are said to be symmetric if they will have identical values for  $S_{12}$  and  $S_{21}$ , together with  $S_{11} = S_{22}$ . For example we would normally expect an attenuator to have the same attenuation for whichever direction the power flows through it, so it would have symmetrical S-parameters.

The product  $S_{12}S_{21}$  is an important quantity in the case of many 2-port networks. If its input port was at port 1,  $S_{21}$  would be a linear measure of what would happen to the signal applied at the input and arriving at the output, port 2. In fact  $S_{21}$  is known as the linear transmission, or linear gain in the case of an amplifier. After the input signal has been amplified (by  $S_{21}$ ) then a proportion of the signal might find its way from the output back to the input again if  $S_{12}$  was non-zero. The product  $S_{12}S_{21}$  is known as the open loop gain, an important parameter to account for if:

- we wish to design an amplifier that will not oscillate;
- we wish to actually design an oscillator.

In fact, transistors are available for oscillators which have designed-in finite  $S_{12}S_{21}$  values.

Transistors for use as amplifiers for be designed with the smallest possible value for  $S_{12}S_{21}$ . A 2-port network is said to be perfectly unilateral if  $S_{12}S_{21}$  is zero. When we connect together several 2-port networks into a cascade, with the output of each network connected to the input of the next, we normally wish each network to be as unilateral as possible to avoid any risks of oscillations or other instabilities.

## 2 Power Gain Definitions

Refer again to Figure 1-1. We are now going to consider cases where the 2-port network under consideration is an amplifier, more specifically a power amplifier. A power amplifier, as its name implies, is one that is designed to increase the RF power of a signal applied at the input. These are probably the most common types of amplifiers which are considered with S-parameters, but other examples are voltage amplifiers and current amplifiers. These have their own idiosyncrasies which we will not get involved with today.

If we buy a power amplifier with *nominal* input and output impedances of, say,  $50 \Omega$ , how sure can we be that it will be sufficiently close to  $50 \Omega$  for us? We might expect it to differ slightly from  $50 \Omega$  but by how much and what can we tolerate happening to the phase? If the input impedance of a *unilateral* amplifier was  $48 + j10 \Omega$  for example, it will give quite a respectable return loss (about 20 dB relative to  $50 \Omega$ ), in fact identical to if the input impedance had been  $48 - j10 \Omega$ . If the impedance of the source was  $48 - j10 \Omega$  and input impedance of the amplifier was  $48 + j10 \Omega$ , that would be a perfect conjugate match. Power would transfer perfectly from the source to the amplifier without any loss. Now suppose that the impedances of the source and amplifier happened to be identical at  $48 + j10 \Omega$ . Because that is not a conjugate match, quite a lot of the power from the source would be reflected. In fact the magnitude of the reflection coefficient at the input, *but relative to the source impedance and not  $50 \Omega$* , would only be 0.208, or a return loss of about 14 dB. That means that the reflected power at the amplifier input would be 14 dB less than the incident power, quite a significant waste, especially if we want to transfer high power.

It is for these type of situations that there are different definitions of power gain. Also you will remember that I conveniently assumed the amplifier to be perfectly unilateral as that approximation saves us lots of trouble. From this point onwards we will assume that the network is bilateral. That is to say that we will allow for signals in both directions so different loadings of the output can affect what is seen at the input, and vice versa.

Here again are the types of power gain that we first met in Section 1.3:

- Power available from the source,  $P_{AVS}$ .
- Input power to the network,  $P_{IN}$ .
- Power available from the network,  $P_{AVN}$ .
- Power dissipated in the load,  $P_L$ .

There are 3 ways of defining power gain with the following (scalar) quantities:

- Operating Power Gain ( $G_{OP} = P_L / P_{IN}$ ).
- Available Power Gain ( $G_A = P_{AVN} / P_{AVS}$ ).
- Transducer Power Gain ( $G_T = P_L / P_{AVS}$ ).

These are described in the following sections.

### 2.1 Operating Power Gain

The operating power gain  $G_{OP}$  is the ratio of the power dissipated in the load  $P_L$  to the power delivered to the input of the 2-port network  $P_{IN}$ , so

$$G_{OP} = \frac{P_L}{P_{IN}} \quad (2.1)$$

## S-Parameters and Power Gain Definitions

From Figure 1-1, if the total voltage at the input: the standing wave which is made up of the forward and reverse waves,  $V_{1+}$  and  $V_{1-}$  respectively, is  $V_1$ , then

$$V_1 = V_{1+} + V_{1-} \quad (2.2)$$

Using the definition of input reflection coefficient in (1.1),

$$\begin{aligned} V_1 &= V_{1+} + V_{1-} \\ &= V_{1+} + \rho_{IN} V_{1+} \\ &= V_{1+} (1 + \rho_{IN}) \end{aligned} \quad (2.3)$$

An alternative way of describing  $V_1$  is in terms of the potential divider action of  $Z_S$  and  $Z_{IN}$  on the voltage at the source  $V_S$ , so

$$V_1 = V_S \left( \frac{Z_{IN}}{Z_S + Z_{IN}} \right) \quad (2.4)$$

Equating (2.3) and (2.4)

$$\begin{aligned} V_S \left( \frac{Z_{IN}}{Z_S + Z_{IN}} \right) &= V_{1+} (1 + \rho_{IN}) \\ V_{1+} &= \left( \frac{V_S}{1 + \rho_{IN}} \right) \left( \frac{Z_{IN}}{Z_S + Z_{IN}} \right) \end{aligned} \quad (2.5)$$

At this point it is useful to get expressions for the source and load impedances,  $Z_S$  and  $Z_L$  related to their associated reflection coefficients  $\rho_S$  and  $\rho_L$  respectively. When we express a reflection coefficient in terms of impedance we need to relate it to a reference impedance and without doubt the most useful would be the same system impedance that we used for the S-parameters,  $Z_0$ . Therefore, for the load,

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (2.6)$$

Re-arranging in terms of the load impedance

$$Z_L = Z_0 \left( \frac{1 + \rho_L}{1 - \rho_L} \right) \quad (2.7)$$

Similarly, for the source and input impedances

$$Z_S = Z_0 \left( \frac{1 + \rho_S}{1 - \rho_S} \right) \quad (2.8)$$

and

## S-Parameters and Power Gain Definitions

$$Z_{IN} = Z_0 \left( \frac{1 + \rho_{IN}}{1 - \rho_{IN}} \right) \quad (2.9)$$

In fact, there are of course similar expressions to (2.6) and (2.7) for all of the other reflection coefficients.

By substitution from (2.8) and (2.9) for  $Z_S$  and  $Z_{IN}$  into (2.5) after a little perseverance we will get the following result

$$V_{1+} = \frac{V_S}{2} \frac{(1 - \rho_S)}{(1 - \rho_S \rho_{IN})} \quad (2.10)$$

Next we call on our study of average power in Section 1.3 and use (1.36) as follows:

$$\begin{aligned} P_{IN} &= \frac{1}{2Z_0} |V_{1+}|^2 (1 - |\rho_{IN}|^2) \\ &= \frac{|V_S|^2}{8Z_0} \frac{|1 - \rho_S|^2}{|1 - \rho_S \rho_{IN}|^2} (1 - |\rho_{IN}|^2) \end{aligned} \quad (2.11)$$

Noting that  $V_{2-}$ , the reflected wave from port 2 is identical to the incident wave at the load, then the power delivered to the load  $P_L$  is, by the same reasoning,

$$P_L = \frac{|V_{2-}|^2}{2Z_0} (1 - |\rho_L|^2) \quad (2.12)$$

A few more stages of quite tedious algebra are still required. From (1.40), in terms of  $V_{2-}$

$$V_{2-} = \frac{S_{21} V_{1+}}{1 - S_{22} \rho_L} \quad (2.13)$$

As the complex numbers are in the form of products and/or quotients, (2.13) can be written in magnitude form as follows

$$|V_{2-}| = \frac{|S_{21}| |V_{1+}|}{|1 - S_{22} \rho_L|} \quad (2.14)$$

Substituting for  $|V_{2-}|$  from (2.13) into (2.12)

$$P_L = \frac{|S_{21}|^2 |V_{1+}|^2 (1 - |\rho_L|^2)}{2Z_0 |1 - S_{22} \rho_L|^2} \quad (2.15)$$

Substituting for  $|V_{1+}|$  from (2.10) into (2.15)

$$P_L = \frac{|S_{21}|^2 (1 - |\rho_L|^2) |V_S|^2 |1 - \rho_S|^2}{8Z_0 |1 - S_{22} \rho_L|^2 |1 - \rho_S \rho_{IN}|^2} \quad (2.16)$$

## S-Parameters and Power Gain Definitions

Substituting for  $P_L$  from (2.16) and for  $P_{IN}$  from (2.11), the operating power gain  $G_{OP}$  is

$$G_{OP} = \frac{P_L}{P_{IN}} = \frac{|S_{21}|^2 (1 - |\rho_L|^2)}{(1 - |\rho_{IN}|^2) |1 - S_{22}\rho_L|^2} \quad (2.17)$$

As this is a power gain it is a ratio of powers, more correctly mean powers, for which we do not normally specify any phase. It is clear from (2.17) that, although they were derived from complex quantities, the coefficients involved are actually all magnitudes so the result  $G_{OP}$  is a scalar quantity.

### 2.2 Available Power Gain

The available power gain  $G_A$  is the ratio of the power available from the 2-port network  $P_{AVN}$  to the power available from the source  $P_{AVS}$ , so

$$G_A = \frac{P_{AVN}}{P_{AVS}} \quad (2.18)$$

The (maximum) power available from the source  $P_{AVS}$  is when it is conjugatively matched to the input of the network. That is, when the input impedance of the network is the conjugate of the source impedance, or

$$\rho_{IN} = \rho_S^* \quad (2.19)$$

Substituting for  $\rho_{IN}$  from (2.19) into (2.11), and remembering that

$$|\rho_S^*|^2 = |\rho_S|^2 \quad (2.20)$$

then

$$\begin{aligned} P_{AVS} &= \frac{|V_S|^2}{8Z_0} \frac{|1 - \rho_S|^2}{|1 - |\rho_S|^2|^2} (1 - |\rho_S^*|^2) \\ &= \frac{|V_S|^2}{8Z_0} \frac{|1 - \rho_S|^2}{(1 - |\rho_S|^2)} \end{aligned} \quad (2.21)$$

Similarly to the source, the power available from the network is equivalent to the maximum power which can be delivered to the load. That is, when  $\rho_{OUT}$  is a conjugate match to the load reflection coefficient  $\rho_L$ , or

$$\rho_L = \rho_{OUT}^* \quad (2.22)$$

Therefore,

$$|\rho_L| = |\rho_{OUT}| \quad (2.23)$$

Substituting from (2.22) and (2.23) into (2.16)

## S-Parameters and Power Gain Definitions

$$P_{AVN} = \frac{|V_S|^2 |S_{21}|^2 (1 - |\rho_{OUT}|^2) |1 - \rho_S|^2}{8Z_0 |1 - S_{22}\rho_{OUT}^*|^2 |1 - \rho_S\rho_{IN}|^2} \quad (2.24)$$

The following step is derived from (1.44)

$$|1 - \rho_S\rho_{IN}|^2 = \frac{|1 - S_{11}\rho_S|^2 (1 - |\rho_{OUT}|^2)^2}{|1 - S_{22}\rho_{OUT}^*|^2} \quad (2.25)$$

Substituting (2.25) into (2.24) gives the result

$$P_{AVN} = \frac{|V_S|^2 |S_{21}|^2 |1 - \rho_S|^2}{8Z_0 |1 - S_{11}\rho_S|^2 (1 - |\rho_{OUT}|^2)} \quad (2.26)$$

By substituting (2.21) and (2.26) into (2.18) the result for the available power gain  $G_A$  is

$$G_A = \frac{P_{AVN}}{P_{AVS}} = \frac{|S_{21}|^2 (1 - |\rho_S|^2)}{|1 - S_{11}\rho_S|^2 (1 - |\rho_{OUT}|^2)} \quad (2.27)$$

### 2.3 Transducer Power Gain

The transducer gain  $G_T$  is the ratio of the power delivered to the load  $P_L$  to the power available from the source  $P_{AVS}$ , therefore

$$G_T = \frac{P_L}{P_{AVS}} \quad (2.28)$$

We already have expressions for  $P_L$  and  $P_{AVS}$  from (2.16) and (2.21) respectively, so the transducer power gain  $G_T$  is

$$G_T = \frac{P_L}{P_{AVS}} = \frac{|S_{21}|^2 (1 - |\rho_S|^2) (1 - |\rho_L|^2)}{|1 - \rho_S\rho_{IN}|^2 |1 - S_{22}\rho_L|^2} \quad (2.29)$$

### 2.4 Comparing the Power Gain Definitions

We have at last derived the expressions for operating power gain  $G_{OP}$  (2.17), available power gain  $G_{AV}$  (2.27) and transducer power gain  $G_T$  (2.29). These are repeated below for convenience

$$G_{OP} = \frac{P_L}{P_{IN}} = \frac{|S_{21}|^2 (1 - |\rho_L|^2)}{(1 - |\rho_{IN}|^2) |1 - S_{22}\rho_L|^2} \quad (2.30)$$

## S-Parameters and Power Gain Definitions

$$G_A = \frac{P_{AVN}}{P_{AVS}} = \frac{|S_{21}|^2 (1 - |\rho_S|^2)}{|1 - S_{11}\rho_S|^2 (1 - |\rho_{OUT}|^2)} \quad (2.31)$$

$$G_T = \frac{P_L}{P_{AVS}} = \frac{|S_{21}|^2 (1 - |\rho_S|^2) (1 - |\rho_L|^2)}{|1 - \rho_S\rho_{IN}|^2 |1 - S_{22}\rho_L|^2} \quad (2.32)$$

Notice again that all three power gain definitions are scalar quantities. This might have been expected since a power waveform, although periodic, is not sinusoidal as it can only have a positive instantaneous value. It does not therefore have a phase associated with it.

If we had a hypothetical system in which all the impedances were exactly equal to  $Z_0$  then, as  $Z_0$  is the system impedance, all of the magnitudes of the reflection coefficients would also be zero. This is implied by (2.6) in the case of  $\rho_L$  and similar other equations for the other reflection coefficients. Therefore, from (2.30), (2.31) and (2.32), for a perfectly matched system,

$$G_{OP} = G_{AV} = G_T = |S_{21}|^2 \quad (2.33)$$


More realistically, the network might be an active device such as a transistor. Provided it is operating linearly and is unconditionally stable at the frequency under consideration, then our discussions are reliable. Today's technology cannot yet produce transistor architectures which have impedances near our most common system impedance of  $50 \Omega$  and maintain them over frequency, so various forms of matching are commonplace.

### 2.5 Power Gains in Practical Systems

Often in communications systems we are faced with needing to insert a *fairly arbitrary 2-port network* into a cascade (or a series chain) of 2-port networks as shown in Figure 2-1. Figure 2-1 (a) shows that, at the beginning of the cascade, there would be some form of source, in this case represented by a Thevenin equivalent circuit with voltage source  $V_A$  and a source impedance  $Z_A$ . At the output of the cascade there would be a load, in this case  $Z_B$ . In general  $Z_A$  and  $Z_B$  are both complex and frequency-dependent. The intermediate stages comprising the cascade may have many different input and output impedances. These may be considered equivalent to a single Thevenin equivalent circuit with source impedance  $Z_S$  at the input and a load of  $Z_L$  at the output. Now suppose we wish to insert a 2-port network  $S_K$  into the cascade, whose S-parameters are already known, as shown in Figure 2-1(b). If it was inserted directly into the cascade, *without any matching*, it would probably not be matched by chance so we could expect some reflected power at either port of the network, probably both.

In this case, if we were interested in how the network affects the overall power gain of the cascade, we would use the definition of transducer power gain  $G_T$  for the network, as defined in (2.32). By using (2.32) we would automatically take into account the mismatches present at the input and output of  $S_K$ . The impedance  $Z_S$  results in the reflection coefficient  $\rho_S$  and similarly for  $Z_L$  and  $\rho_L$ .


## S-Parameters and Power Gain Definitions

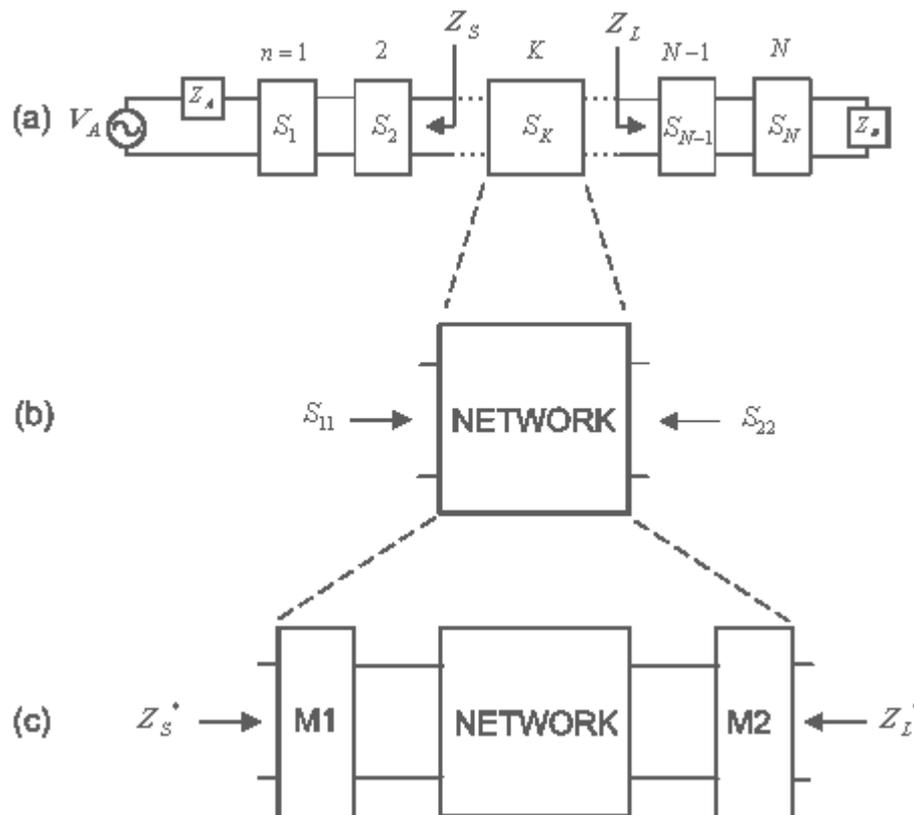

**Figure 2-1** A schematic showing two ways of substituting a 2-port network into a cascade: unmatched (a) and simultaneously conjugately matched (b)

### 2.5.1 Matching for Maximum Power Transfer

By inserting the network  $S_K$  into the cascade as we did in Section 2.5, we did not make the assumption that  $S_K$  was unilateral. In other words, we are not assuming that we can simply match the input with a source impedance of  $S_{11}^*$  and the output with a load impedance of  $S_{22}^*$ . The S-parameters of the network were measured stand-alone using a system impedance  $Z_0$  which is not necessarily anything like those we are trying to match to. In a network such as this which may not be unilateral, when it is inserted into the cascade, the impedance seen at the input may be affected by the output loading. Similarly the impedance seen at the output may be affected by the input or source loading. We would need to use (1.44) or (1.45) to determine the actual input impedance or output impedance.

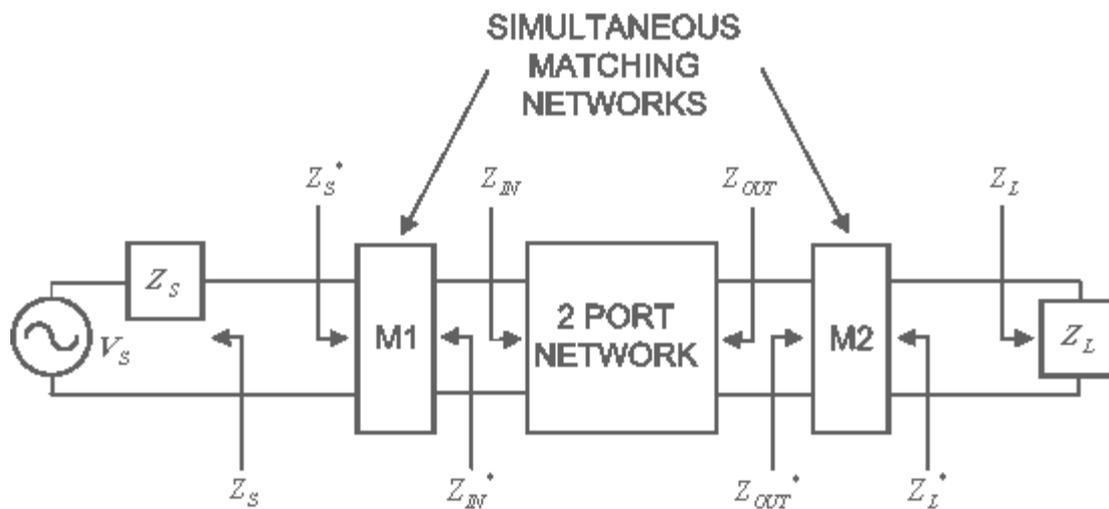

**Figure 2-2 A generic 2-port network that is simultaneously conjugately matched to a source and load**

To maximise the power transmitted along the cascade, one solution would be to design simultaneous input and output matching for the network  $S_K$  [8]. This is shown in Figure 2-1(c) and with more detail in Figure 2-2. M1 and M2 are matching networks positioned respectively at the input and output of the network  $S_K$  and they are designed to ensure that each input and output impedance seen is matched by a conjugate match in the opposite direction. The impedances and their conjugates are shown in Figure 2-2. In practice there are several prerequisites for matching of this type to work successfully, the most challenging requiring M1 and M2 to be sufficiently low loss across the intended operating frequency range.

One successfully designed this form of matching will ensure that power is efficiently transferred from input to output and will be equivalent to the result in (2.33).

### 3 References

1. Pozar, David M.; *Microwave Engineering – Third Edition*, John Wiley & Sons Inc.; pp 536 – 539. ISBN 0-471-44878-8 (2005).
2. Gonzalez, Guillermo; *Microwave Transistor Amplifiers, Analysis and Design – Second Edition*; Prentice-Hall Inc., Upper Saddle River, NJ 07458. ISBN 0-13-254335-4 (1984).
3. Ramo, Simon; Whinnery, John R.; Van Duzer, Theodore; *Fields and waves in Communications Electronics*; John Wiley & Sons, New York; pp 603 – 604.
4. *S-Parameter Design*; Agilent Application Note AN 154.
5. *S-Parameter Techniques for Faster, More Accurate Network Design*; HP Test and Measurement Application Note AN 95-1.
6. Pozar (op. cit); pp 539 – 540.
7. Vendelin, George D.; *Design of Amplifiers and Oscillators by the S-Parameter Method*; John Wiley & Sons (1982).
8. Pozar (op.cit); pp 548 – 551.
9. Kreyszig, Erwin; *Advanced Engineering Mathematics, Fourth Edition*; John Wiley & Sons (1979); pp 589 – 591.
10. Ramo, Whinnery & Van Duzer; *Fields and Waves in Communications Electronics*; John Wiley & Sons (1965); pp 31 – 34.